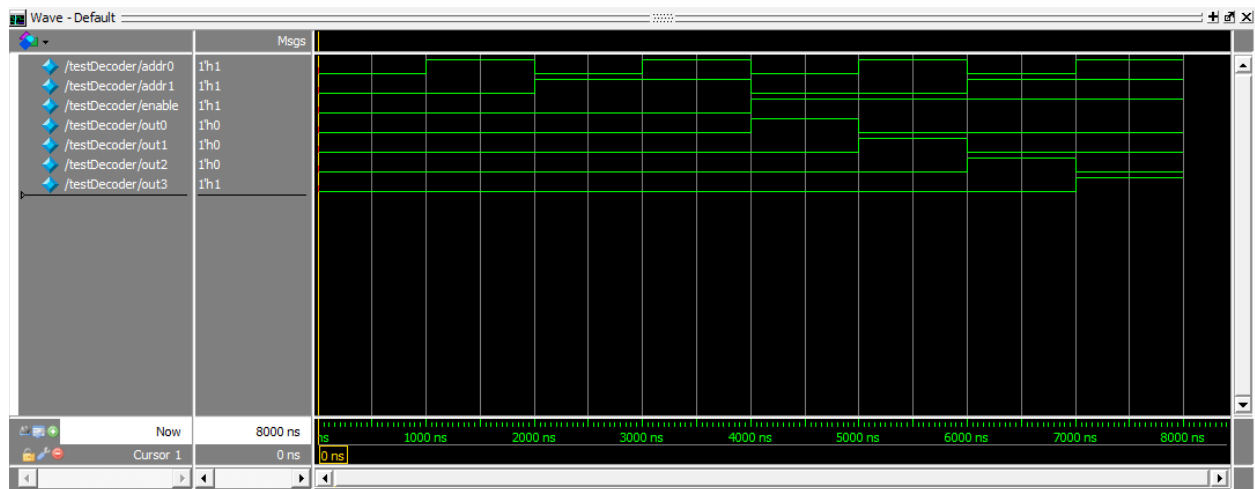


# Computer Architecture HW2 RESULTS

Brenna Manning


## Decoder Waveform:



## Decoder Test Bench Results:

```
# Loading work.testDecoder
# Loading work.structuralDecoder
# En A0 A1| O0 O1 O2 O3 | Expected Output
# 0 0 0 | 0 0 0 0 | All false
# 0 1 0 | 0 0 0 0 | All false
# 0 0 1 | 0 0 0 0 | All false
# 0 1 1 | 0 0 0 0 | All false
# 1 0 0 | 1 0 0 0 | O0 Only
# 1 1 0 | 0 1 0 0 | O1 Only
# 1 0 1 | 0 0 1 0 | O2 Only
# 1 1 1 | 0 0 0 1 | O3 Only
```

## Full Adder Waveform:

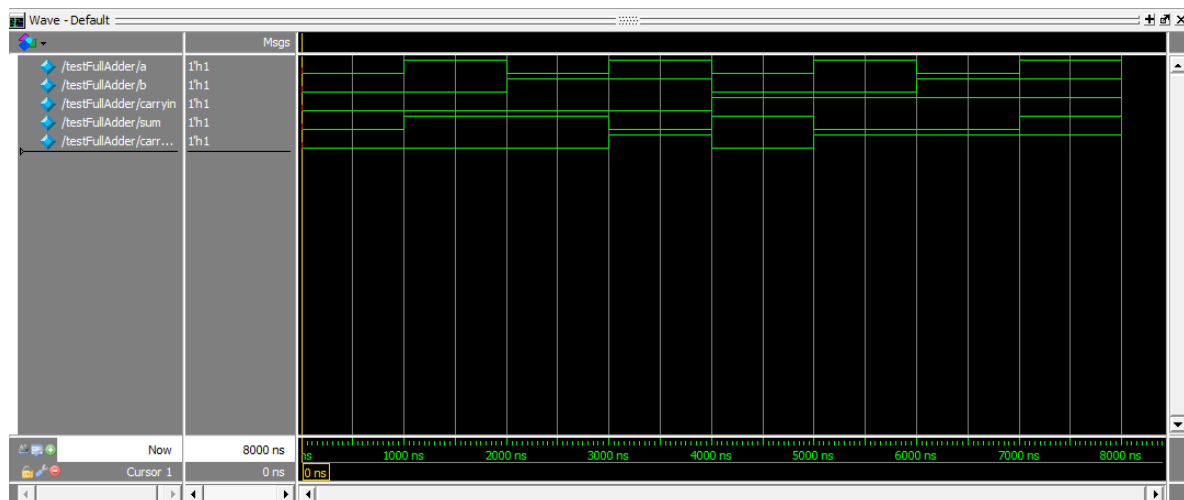


## Computer Architecture HW2 RESULTS

Brenna Manning

### Full Adder Test Bench Results:

```
# Loading work.testFullAdder
# Loading work.structuralFullAdder
# A B  CIn|Sum COut| Expected Output
# 0 0 0 | 0 0 | 0 0
# 1 0 0 | 1 0 | 1 0
# 0 1 0 | 1 0 | 1 0
# 1 1 0 | 0 1 | 0 1
# 0 0 1 | 1 0 | 1 0
# 1 0 1 | 0 1 | 0 1
# 0 1 1 | 0 1 | 0 1
# 1 1 1 | 1 1 | 1 1
```

### Multiplexer Waveform:

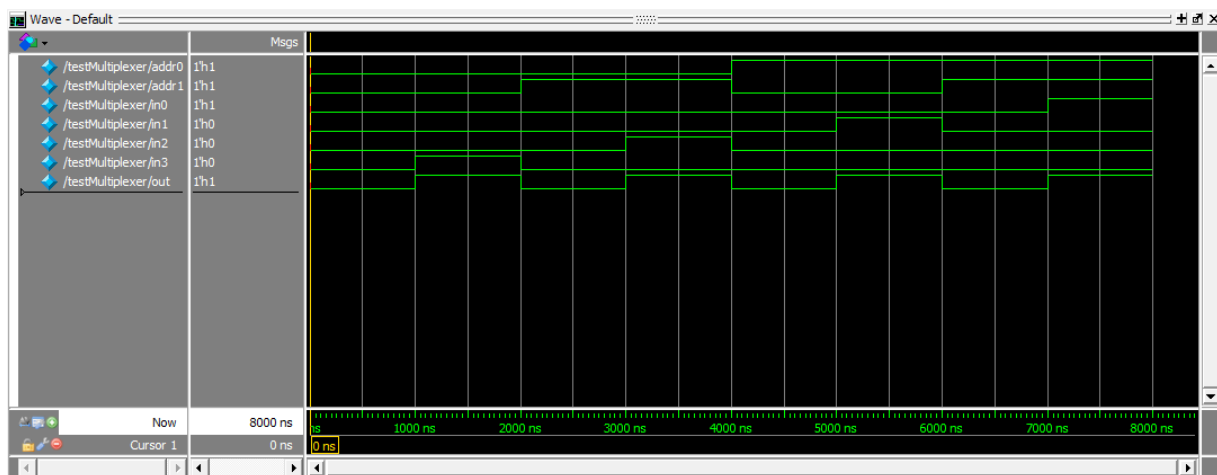

### Multiplexer Test Bench Results:

```
# Loading work.testMultiplexer
# Loading work.structuralMultiplexer
# A0 A1 In0 In1 In2 In3 | Out | Expected Output
# 0 0 0 0 0 0 | 0 | 0
# 0 0 0 0 0 1 | 1 | 1
# 0 1 0 0 0 0 | 0 | 0
# 0 1 0 0 1 0 | 1 | 1
# 1 0 0 0 0 0 | 0 | 0
# 1 0 0 1 0 0 | 1 | 1
# 1 1 0 0 0 0 | 0 | 0
# 1 1 1 0 0 0 | 1 | 1
```